


1

(a) Define the capacitance of a capacitor.


charge stored per volt  
 $C = \frac{Q}{V}$

(2)

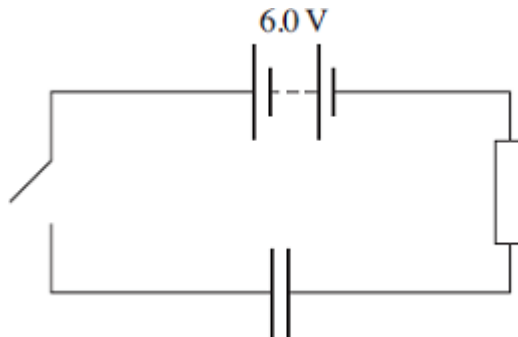(b) The circuit shown in the figure below contains a battery, a resistor, a capacitor and a switch.



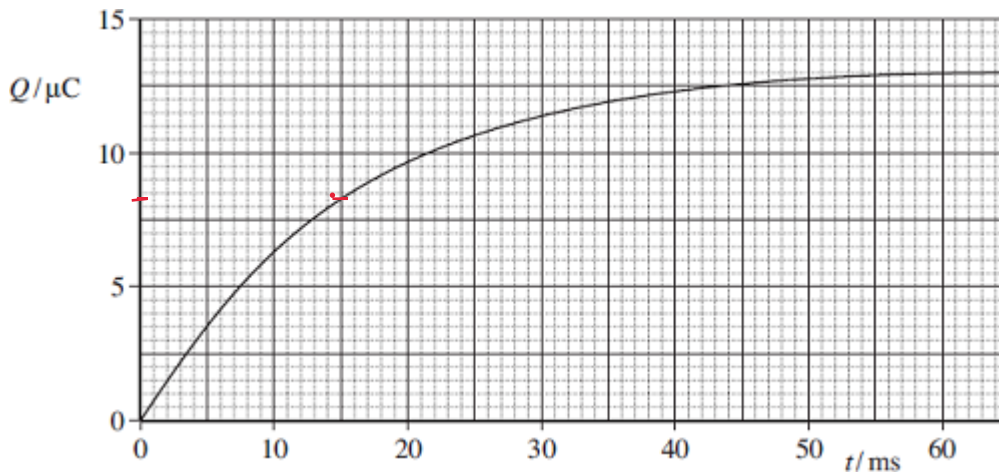The switch in the circuit is closed at time  $t = 0$ . The graph shows how the charge  $Q$  stored by the capacitor varies with  $t$ .



(b) (i) When the capacitor is fully charged, the charge stored is  $13.2 \mu\text{C}$ . The electromotive force (emf) of the battery is  $6.0 \text{ V}$ . Determine the capacitance of the capacitor.

$$C = \frac{Q}{V} = \frac{13.2 \times 10^{-6}}{6}$$

answer =  $2.2 \times 10^{-6} \text{ F}$

(2)

- (ii) The time constant for this circuit is the time taken for the charge stored to increase from 0 to 63% of its final value. Use the graph to find the time constant in milliseconds.

$$13.2 \times 0.63 = 8.3$$

answer = 15 ms

(2)

- (iii) Hence calculate the resistance of the resistor.

$$\frac{\text{Time Constant}}{2.2 \times 10^{-6}} = RC$$

answer =  $6.8 \times 10^3$   $\Omega$

(1)

- (iv) What physical quantity is represented by the gradient of the graph?

Current (change in Q/t)

(1)


- (c) (i) Calculate the maximum value of the current, in mA, in this circuit during the charging process.

$$\frac{V}{R} = I \Rightarrow I = \frac{6}{6.8k} =$$

answer = 0.9 (0.88) mA

(1)

- (ii) Sketch a graph on the outline axes to show how the current varies with time as the capacitor is charged. Mark the maximum value of the current on your graph.

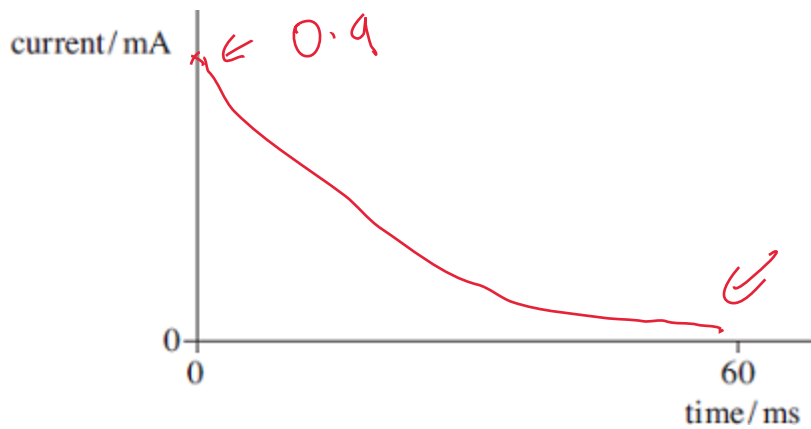

approaches 0  
∴ 4  
time constants

(2)

(Total 11 marks)


2

- (a) State the **three** factors upon which the capacitance of a parallel plate capacitor depends.

*A of plates that are parallel  
d between plates  
material of dielectric*

(2)

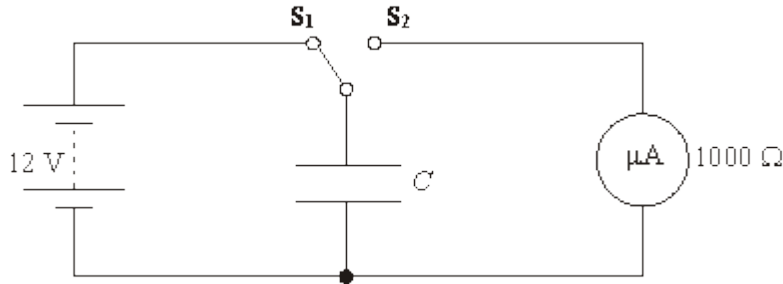- (b) The figure below shows a circuit for measuring the capacitance of a capacitor.



The switch is driven by a signal generator and oscillates between **S<sub>1</sub>** and **S<sub>2</sub>** with frequency  $f$ .

When the switch is in position **S<sub>1</sub>** the capacitor charges until the potential difference across it is equal to the supply emf. When the switch moves to position **S<sub>2</sub>** the capacitor discharges through the microammeter which has a resistance of  $1000\ \Omega$ .

In one experiment a  $0.047\ \mu\text{F}$  capacitor is used with a  $12\ \text{V}$  supply.

- (i) Calculate the charge stored by the capacitor when the switch is in position **S<sub>1</sub>**.

$$Q = CV = 0.047 \times 10^{-6} \times 12 = \underline{5.64 \times 10^{-7}\ \text{C}}$$

(2)

- (ii) Calculate the time for which the switch must remain in contact with **S<sub>2</sub>** in order for the charge on the capacitor to fall to 1% of its initial charge.

$$Q = Q_0 e^{-t/RC} \Rightarrow \frac{Q}{Q_0} = e^{-t/RC} \Rightarrow \ln\left(\frac{Q}{Q_0}\right) = -\frac{t}{RC}$$

$$RC \ln\left(\frac{1}{100}\right) = -t$$

$$1000 \times 0.047 \times 10^{-6} \times \ln(0.01) = -t$$

$$2.2 \times 10^{-4}\ \text{s}$$

(3)

- (iii) Assuming that the capacitor discharges all the stored charge through the microammeter, calculate the reading on the meter when the switch oscillates at 400 Hz.

$$400 \times 5.6 \times 10^{-7} = \underline{0.22 \text{ mA}}$$

(1)

(Total 8 marks)

3

A capacitor of capacitance  $C$  has a charge of  $Q$  stored on the plates. The potential difference between the plates is doubled.

What is the change in the energy stored by the capacitor?

- A  $\frac{Q^2}{2C}$
- B  $\frac{Q^2}{C}$
- C  $\frac{3Q^2}{2C}$
- D  $\frac{2Q^2}{C}$

$$E = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} QV = \frac{1}{2} CV^2$$

double  $V$  the  $Q$  &  $d$  double

$$\text{So } E' = \frac{1}{2} \frac{(2Q)^2}{C} = \frac{1}{2} \frac{4Q^2}{C} = 2 \frac{Q^2}{C}$$

$$\Delta E = E' - E = 2 \frac{Q^2}{C} - \frac{1}{2} \frac{Q^2}{C} = \frac{Q^2}{C} \left( 2 - \frac{1}{2} \right) = \frac{3Q^2}{2C}$$

(Total 1 mark)

4

A parallel-plate capacitor has square plates of length  $l$  separated by distance  $d$  and is filled with a dielectric.

A second capacitor has square plates of length  $2l$  separated by distance  $2d$  and has air as its dielectric.

Both capacitors have the same capacitance.

What is the relative permittivity of the dielectric in the first capacitor?

- A  $\frac{1}{2}$
- B 1
- C 2
- D 8

$$\frac{\cancel{l^2} \epsilon_r}{d} = \frac{2^2 \cancel{l^2} \epsilon_0}{2d}$$

$$C_1 = \frac{l^2 \epsilon_0 \epsilon_r}{d}$$

$$C_1 = C_2$$

$$C_2 = \frac{(2l)^2 \epsilon_0 \epsilon_r}{2d} = \frac{4l^2 \epsilon_0}{2d}$$

$$C_2 = \frac{2l^2 \epsilon_0}{d}$$

(Total 1 mark)

**5**

A parallel-plate capacitor is fully charged and then disconnected from the power supply. A dielectric is then inserted between the plates.

Which row correctly identifies the charge on the plates and the electric field strength between the plates?

	Charge	Electric field strength	
<b>A</b>	Stays the same	Increases	<input type="radio"/>
<b>B</b>	Increases	Decreases	<input type="radio"/>
<b>C</b>	Increases	Increases	<input type="radio"/>
<b>D</b>	Stays the same	Decreases	<input checked="" type="radio"/>

(Total 1 mark)

- There's no more charge to go on plates so stay the same
- The dipoles in dielectric effectively cancel out some of the potential, so decrease

## Mark schemes

1

- (a) charge (stored) ✓ per unit potential difference ✓

[or  $C = Q/V$  where  $Q =$  charge (stored by one plate) ✓  $V =$  pd (across plates) ✓]

2

- (b) (i)  $C \left( = \frac{Q}{V} \right) = \frac{13.2 \times 10^{-6}}{6.0} \checkmark = 2.2 \times 10^{-6} \text{ (F)} \checkmark$  (or 2.2  $\mu\text{F}$ )

2

- (ii) when  $t =$  time constant  $Q = 0.63 \times 13.2 = 8.3 \text{ (}\mu\text{C)} \checkmark$

[or  $= 0.63 \times 13(.0)$  (from graph)  $= 8.2 \text{ (}\mu\text{C)}$ ]

reading from graph gives time constant  $= 15 (\pm 1) \text{ (ms)} \checkmark$

2

- (iii) resistance of resistor  $= \left( = \frac{\text{time constant}}{C} \right) = \frac{15 \times 10^{-3}}{2.2 \times 10^{-6}} = 6820 \text{ (}\Omega) \checkmark$

1

- (iv) gradient = current ✓

1

- (c) (i) maximum current  $= \left( = \frac{V}{R} \right) = \frac{6.0}{6820} = 0.88 \text{ (mA)} \checkmark$

[or value from initial gradient of graph: allow 0.70 – 1.00 mA for this approach]

1

- (ii) curve starts at marked  $I_{\text{max}}$  on  $I$  axis and has decreasing negative gradient ✓

line is asymptotic to  $t$  axis and approaches  $\approx 0$  by  $t = 60 \text{ ms} \checkmark$

2

[11]

2

- (a) area of overlap of the plates

B1

separation of/distance between the plates

permittivity/dielectric constant of free space/the material/dielectric between the plates (condone of the gap)

B1

2

B1 for 1 factor clearly stated

B1 for other two clearly stated

(b) (i)  $Q = VC$  (any form) or  $0.047 \mu\text{F} \times 12$   
(ignoring powers of 10)

C1

$$5.6(4) \times 10^{-7} \text{ C (0.56 } \mu\text{C)}$$

A1

(ii) time constant =  $4.7 \times 10^{-5} \text{ s}$  or  $0.01 = e^{-t/RC}$

C1

$$0.01 = e^{-t/(0.000047)} \text{ or } 0.01 = e^{-t/47} \text{ or } = \frac{t}{RC} = 4.605$$

C1

$$2.2 (2.16) \times 10^{-4} \text{ s or } 0.22 \text{ ms}$$

A1

(iii) their (i)  $\times 400$  (230 (226)  $\mu\text{A}$  or  $2.3 \times 10^{-4} \text{ A}$  if correct)

B1

6

[8]

3 C

[1]

4 C

[1]

5 D

[1]