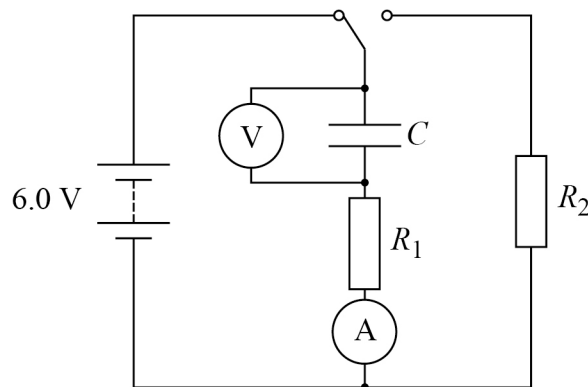


0 5

**Figure 8** shows a circuit used to investigate the charge and discharge of a capacitor of capacitance  $C$  using resistors of resistances  $R_1$  and  $R_2$ .

Figure 8



The battery has an emf of 6.0 V and negligible internal resistance.

0 5 . 1

Show that the time taken for the capacitor to charge from 2.0 V to 4.0 V is approximately  $0.7R_1C$ .

[3 marks]

$$\frac{V}{V_0} = 1 - e^{-\frac{t}{RC}} \Rightarrow \frac{V}{V_0} + e^{-\frac{t}{RC}} = 1 \Rightarrow 1 - \frac{V}{V_0} = e^{-\frac{t}{RC}}$$

$$\ln\left(1 - \frac{V}{V_0}\right) = -\frac{t}{RC}$$

$t_2$  = time to 4V,  $t_1$  = time to 2V and so we want  $t_2 - t_1$

$$t_2: \ln\left(1 - \frac{4}{6}\right) = -\frac{t_2}{R_1C} \Rightarrow t_2 = -R_1C \left(\ln \frac{2}{6}\right)$$

$$\Delta t_1 = -R_1C \left(1 - \frac{2}{6}\right) - \quad \leftarrow \text{double neg}$$

$$\text{so } t_2 - t_1: -R_1C \ln\left(\frac{2}{6}\right) + R_1C \left(\ln \frac{2}{3}\right)$$

$$R_1C \left(\ln \frac{2}{3} - \ln \frac{1}{3}\right) = 0.60 R_1C$$

Question 5 continues on the next page

Turn over ►




The capacitor is fully discharged.

The capacitor is then charged until the potential difference (pd) across it is 4.0 V.

**Figure 9** shows the variation with time of the ammeter reading as the capacitor is charged.

**Figure 9**

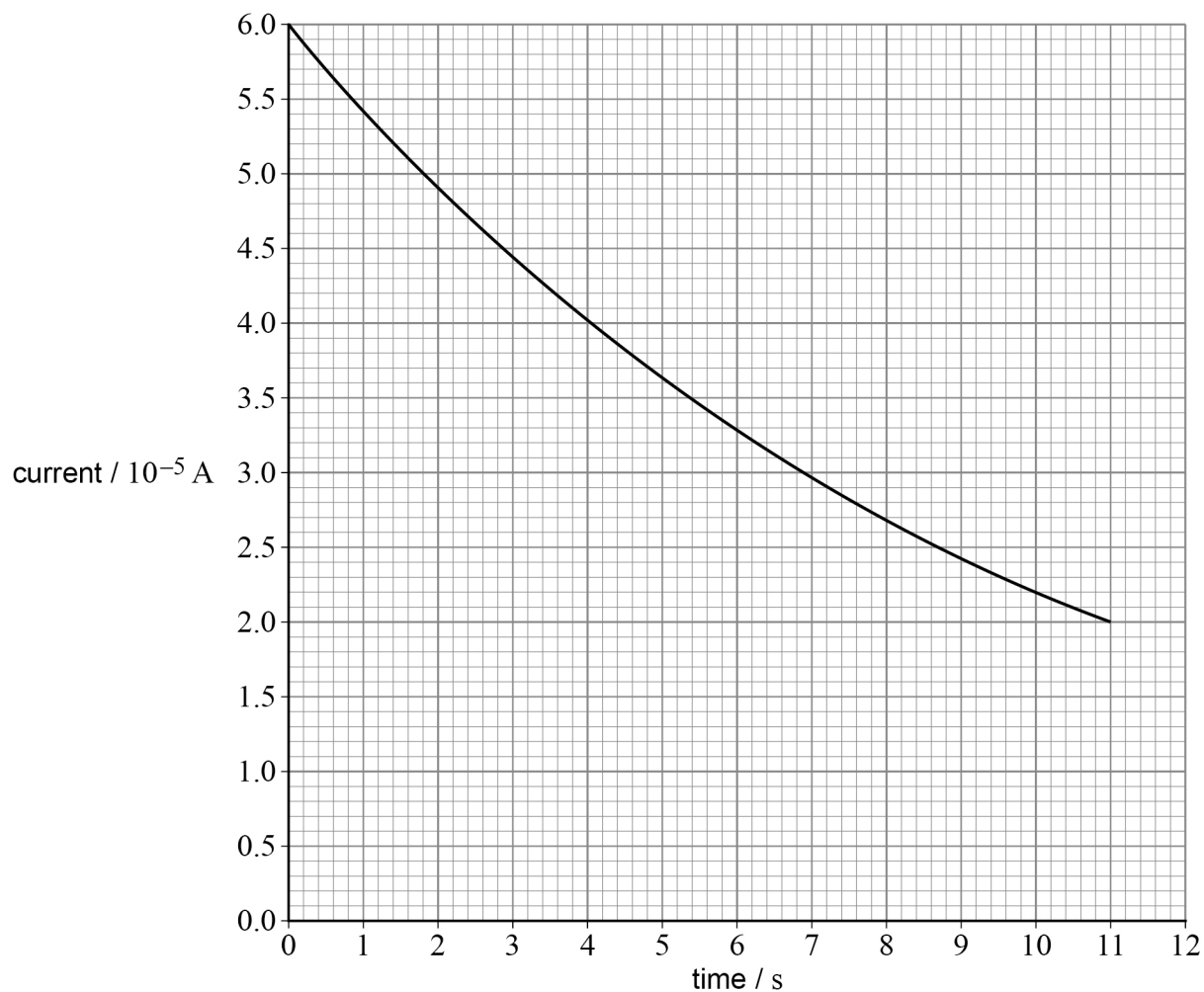

$$\frac{V}{V_0} = e^{-t/RC} \Rightarrow \ln\left(\frac{V}{V_0}\right) = -\frac{t}{RC}$$

$$\text{Find } RC \text{ using } \ln\left(\frac{2}{6}\right) = -\frac{11}{RC}$$

$$\Rightarrow RC = \frac{-11}{\ln\left(\frac{2}{6}\right)} = 8.9 \text{ s}$$

P.T.O



0 5 . 2 Show that the capacitance of the capacitor is about  $1 \times 10^{-4}$  F.

[4 marks]

Get R from  $I_0 = 6 \times 10^{-5}$  A

$V = 60$        $\frac{V}{I} = R \Rightarrow$

$R = 1 \times 10^5 \Omega$

$RC = 8.91 = 1 \times 10^5 \times C$

$\therefore C = 8.9 \times 10^{-5}$

$\approx 1 \times 10^{-4} \text{ F}$

Question 5 continues on the next page

Turn over ►




0 5 . 3

When the pd reaches 4.0 V the switch is immediately set to discharge the capacitor. When the pd reaches 2.0 V the switch is immediately set to charge the capacitor.

Figure 10 shows how the pd across the capacitor varies with time.


Figure 10

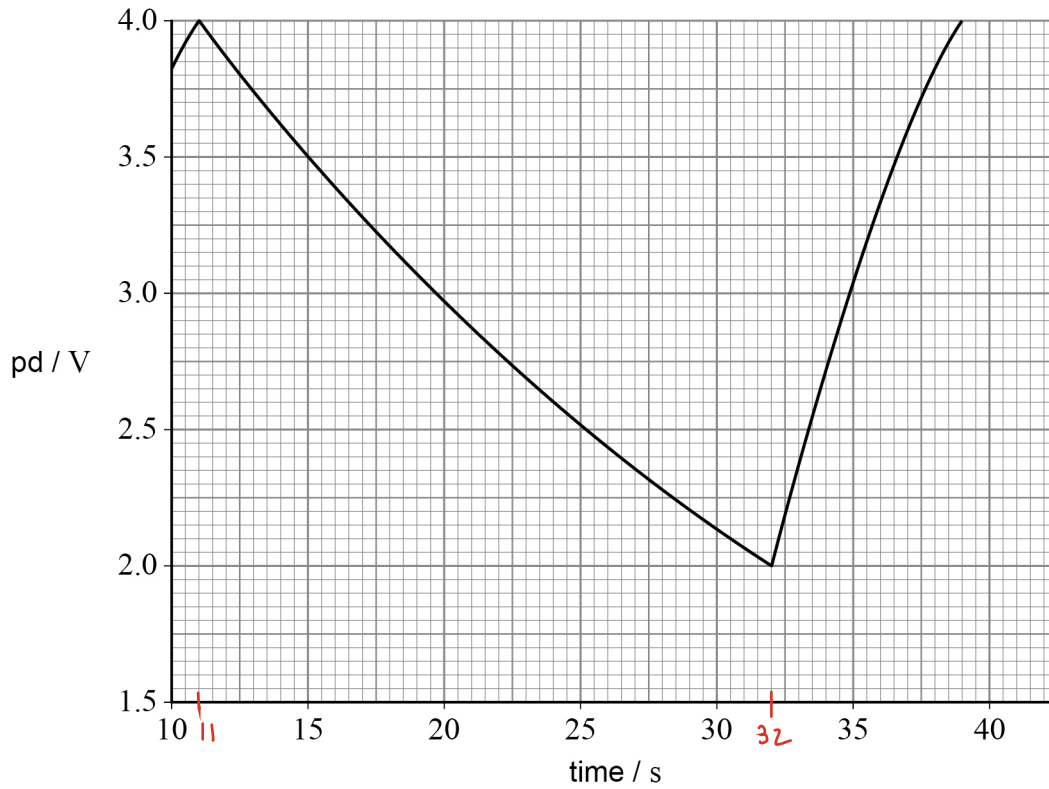

Determine the value of  $R_2$ .

Figure 8

[3 marks]

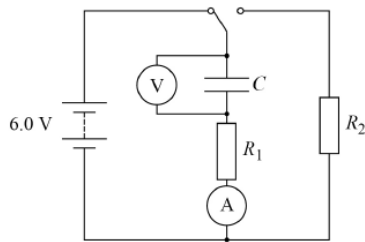

capacitor discharges through  $R_1$

need  $RC$ .  $T = 32 - 11 = 21 \text{ sec}$   
for  $V$  from 4 to 2

$$\frac{V}{V_0} = \frac{1}{2} = e^{-\frac{t}{RC}} \Rightarrow \ln\left(\frac{1}{2}\right) = \frac{-21}{RC} \Rightarrow RC = 30.3 \text{ s}$$

$$RC = 8.9 \times 10^{-5} \times R = 30.3 \Rightarrow R = 3.4 \times 10^5 \Omega$$

total  $\rightarrow \therefore R_2 = 3.4 \times 10^5 - 1 \times 10^5$

$$R_2 = 2.4 \times 10^5 \Omega$$

10




1 7


A switch **S** allows capacitor **C** to be completely charged by a cell and then completely discharged through an ammeter.

The emf of the cell is 4.0 V and it has negligible internal resistance.

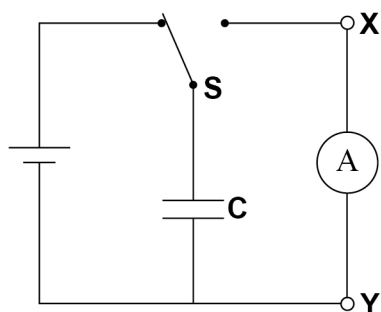The capacitance of **C** is 0.40  $\mu\text{F}$  and there are 8000 charge–discharge cycles every second.



charging

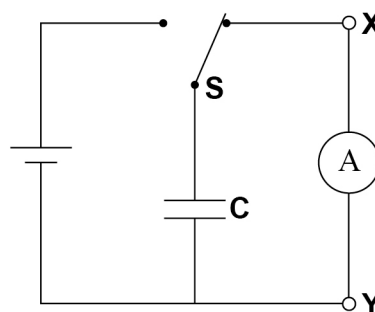

discharging

What are the magnitude and direction of the average conventional current in the ammeter?

[1 mark]

	Magnitude of current / A	Direction of current	
<b>A</b>	$1.3 \times 10^{-2}$	<b>X to Y</b>	<input type="checkbox"/>
<b>B</b>	$1.3 \times 10^{-2}$	<b>Y to X</b>	<input type="checkbox"/>
<b>C</b>	$2.0 \times 10^{-10}$	<b>X to Y</b>	<input type="checkbox"/>
<b>D</b>	$2.0 \times 10^{-10}$	<b>Y to X</b>	<input type="checkbox"/>



**1 8**

A  $30\ \mu\text{F}$  capacitor is charged by connecting it to a battery of emf  $4.0\ \text{V}$ .  
The initial charge on the capacitor is  $Q_0$ .

The capacitor is then discharged through a  $500\ \text{k}\Omega$  resistor.  
The time constant for the circuit is  $T$ .

Which is correct?

**[1 mark]**

**A**  $T$  is  $15\ \text{ms}$ .

**B**  $Q_0$  is  $12\ \mu\text{C}$ .

**C** After a time  $T$  the pd across the capacitor is  $1.5\ \text{V}$ .

**D** After a time  $2T$  the charge on the capacitor is  $Q_0 e^2$ .

**1 9**

Capacitor **X** of capacitance  $C$  has square plates of side length  $l$  and separation  $d$  and is made with a dielectric of relative permittivity  $\epsilon$ .

Capacitor **Y** has square plates of side length  $3l$  and separation  $\frac{d}{3}$  and is made with a

dielectric of relative permittivity  $\frac{\epsilon}{3}$ .

What is the capacitance of **Y**?

**[1 mark]**

**A**  $\frac{C}{27}$

**B**  $\frac{C}{9}$

**C**  $9C$

**D**  $27C$

**Turn over ►**

**2 0**

A parallel plate capacitor is connected across a battery and the energy stored in the capacitor is  $E$ .

Without disconnecting the battery, the separation of the plates is halved.

What is the energy now stored in the capacitor?

**[1 mark]****A**  $0.5E$ **B**  $E$ **C**  $2E$ **D**  $4E$ **2 1**

A fully charged capacitor of capacitance  $2.0 \text{ mF}$  discharges through a  $15 \text{ k}\Omega$  resistor.

What fraction of the stored energy remains after  $1.0 \text{ minute}$ ?

**[1 mark]****A**  $\frac{1}{4}$ **B**  $\frac{1}{e^2}$ **C**  $\frac{1}{16}$ **D**  $\frac{1}{e^4}$ **2 2**

A horizontal wire of length  $0.25 \text{ m}$  carrying a current of  $3.0 \text{ A}$  is perpendicular to a magnetic field. The mass of the wire is  $3.0 \times 10^{-3} \text{ kg}$  and the weight of the wire is supported in equilibrium by the magnetic field.

What is the flux density of the magnetic field?

**[1 mark]****A**  $2.6 \text{ T}$ **B**  $3.9 \times 10^{-2} \text{ T}$ **C**  $2.2 \times 10^{-2} \text{ T}$ **D**  $4.0 \times 10^{-3} \text{ T}$ 