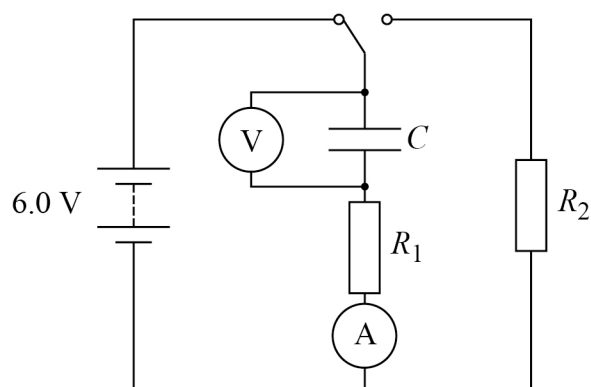


0 5

Figure 8 shows a circuit used to investigate the charge and discharge of a capacitor of capacitance C using resistors of resistances R_1 and R_2 .

Figure 8

The battery has an emf of 6.0 V and negligible internal resistance.

0 5 . 1

Show that the time taken for the capacitor to charge from 2.0 V to 4.0 V is approximately $0.7R_1C$.

[3 marks]

Question 5 continues on the next page

Turn over ►




The capacitor is fully discharged.

The capacitor is then charged until the potential difference (pd) across it is 4.0 V.

Figure 9 shows the variation with time of the ammeter reading as the capacitor is charged.

Figure 9

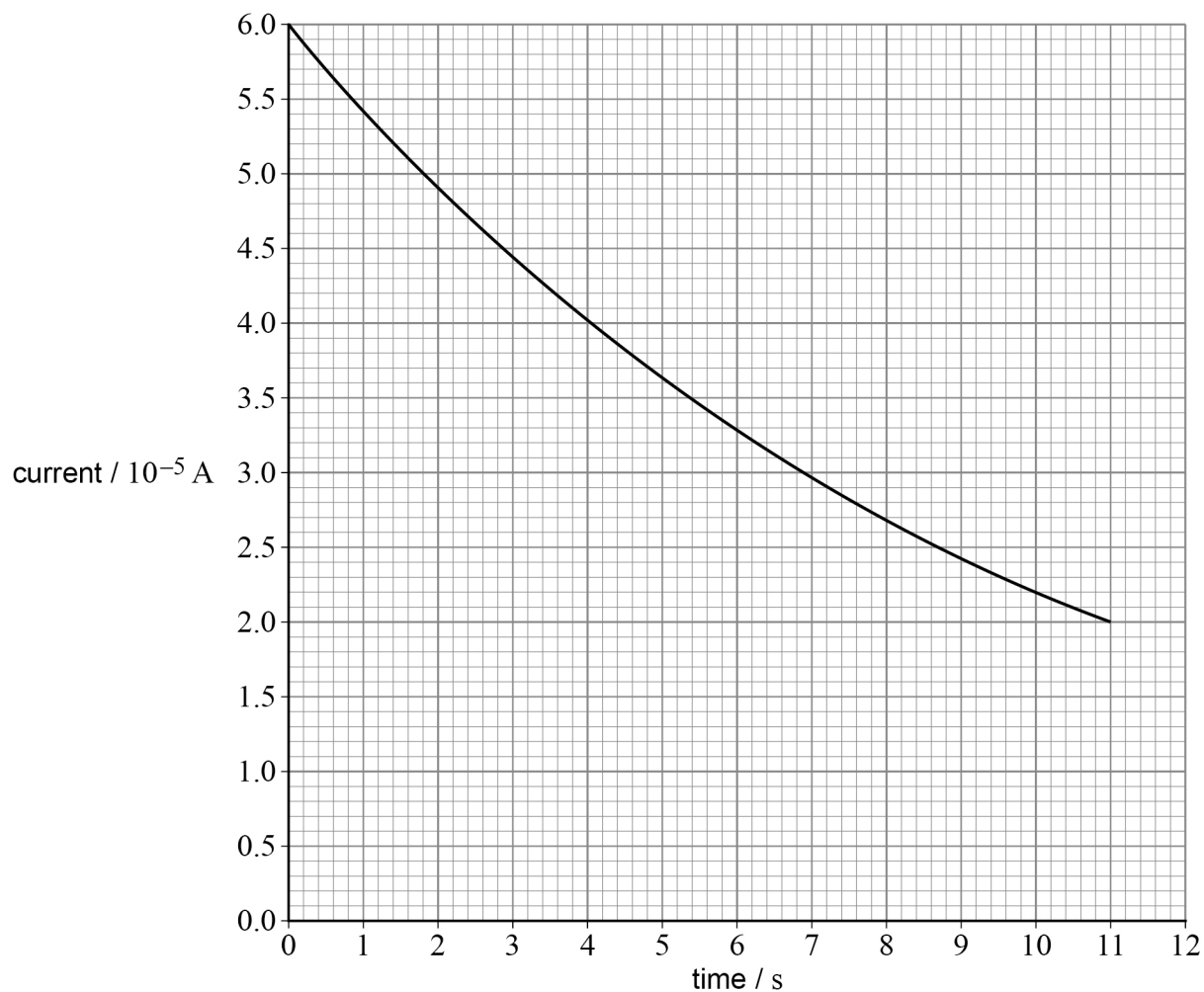

0 5 . 2 Show that the capacitance of the capacitor is about 1×10^{-4} F.

[4 marks]

Question 5 continues on the next page

Turn over ►




0 5 . 3

When the pd reaches 4.0 V the switch is immediately set to discharge the capacitor.
When the pd reaches 2.0 V the switch is immediately set to charge the capacitor.

Figure 10 shows how the pd across the capacitor varies with time.

Figure 10

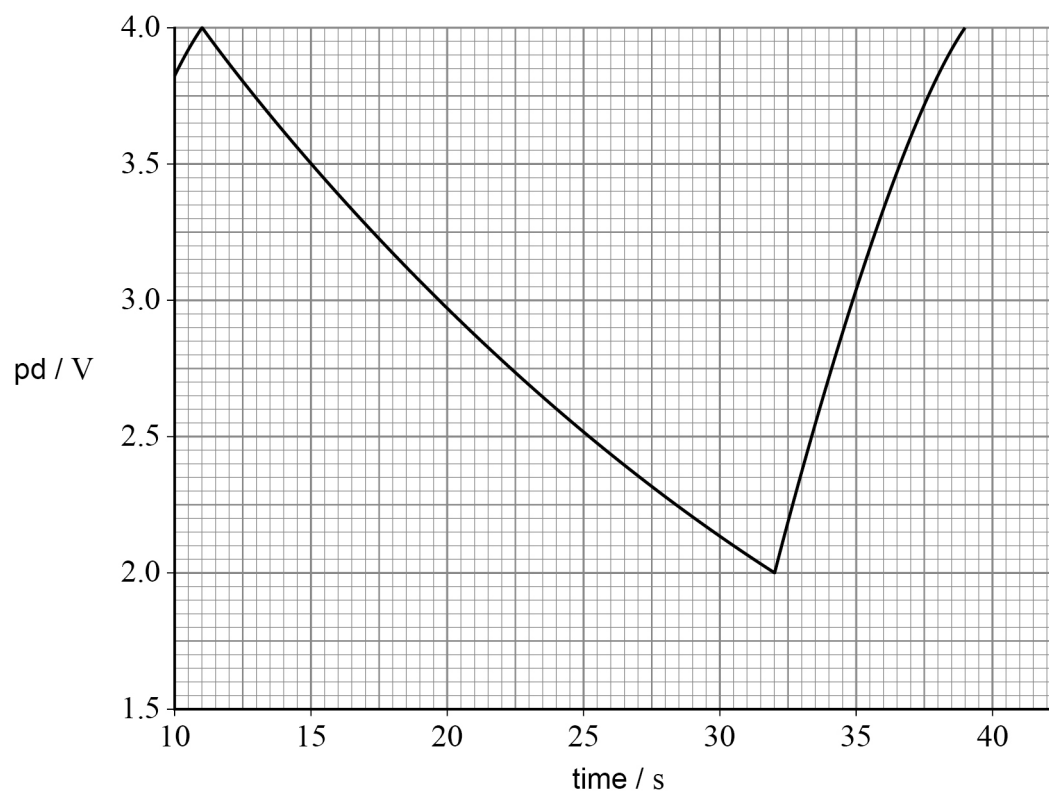

Determine the value of R_2 .

[3 marks]

$R_2 =$ _____ Ω

10




1 7


A switch **S** allows capacitor **C** to be completely charged by a cell and then completely discharged through an ammeter.

The emf of the cell is 4.0 V and it has negligible internal resistance.

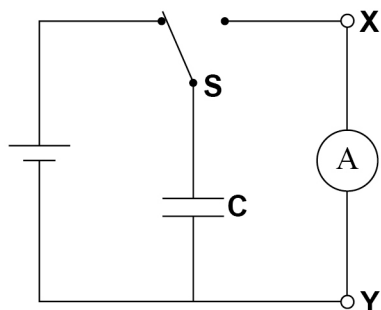The capacitance of **C** is $0.40 \mu\text{F}$ and there are 8000 charge–discharge cycles every second.



charging

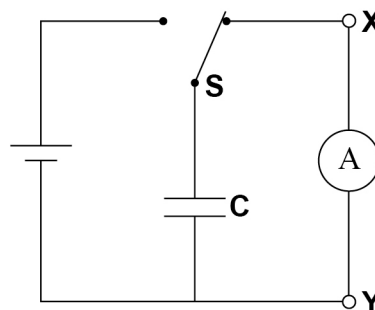

discharging

What are the magnitude and direction of the average conventional current in the ammeter?

[1 mark]

	Magnitude of current / A	Direction of current	
A	1.3×10^{-2}	X to Y	<input type="checkbox"/>
B	1.3×10^{-2}	Y to X	<input type="checkbox"/>
C	2.0×10^{-10}	X to Y	<input type="checkbox"/>
D	2.0×10^{-10}	Y to X	<input type="checkbox"/>



1 8

A $30\ \mu\text{F}$ capacitor is charged by connecting it to a battery of emf $4.0\ \text{V}$.
The initial charge on the capacitor is Q_0 .

The capacitor is then discharged through a $500\ \text{k}\Omega$ resistor.
The time constant for the circuit is T .

Which is correct?

[1 mark]

A T is $15\ \text{ms}$.

B Q_0 is $12\ \mu\text{C}$.

C After a time T the pd across the capacitor is $1.5\ \text{V}$.

D After a time $2T$ the charge on the capacitor is $Q_0 e^2$.

1 9

Capacitor **X** of capacitance C has square plates of side length l and separation d and is made with a dielectric of relative permittivity ϵ .

Capacitor **Y** has square plates of side length $3l$ and separation $\frac{d}{3}$ and is made with a

dielectric of relative permittivity $\frac{\epsilon}{3}$.

What is the capacitance of **Y**?

[1 mark]

A $\frac{C}{27}$

B $\frac{C}{9}$

C $9C$

D $27C$

Turn over ►

2 0

A parallel plate capacitor is connected across a battery and the energy stored in the capacitor is E .

Without disconnecting the battery, the separation of the plates is halved.

What is the energy now stored in the capacitor?

[1 mark]**A** $0.5E$ **B** E **C** $2E$ **D** $4E$ **2 1**

A fully charged capacitor of capacitance 2.0 mF discharges through a $15 \text{ k}\Omega$ resistor.

What fraction of the stored energy remains after 1.0 minute ?

[1 mark]**A** $\frac{1}{4}$ **B** $\frac{1}{e^2}$ **C** $\frac{1}{16}$ **D** $\frac{1}{e^4}$ **2 2**

A horizontal wire of length 0.25 m carrying a current of 3.0 A is perpendicular to a magnetic field. The mass of the wire is $3.0 \times 10^{-3} \text{ kg}$ and the weight of the wire is supported in equilibrium by the magnetic field.

What is the flux density of the magnetic field?

[1 mark]**A** 2.6 T **B** $3.9 \times 10^{-2} \text{ T}$ **C** $2.2 \times 10^{-2} \text{ T}$ **D** $4.0 \times 10^{-3} \text{ T}$ 