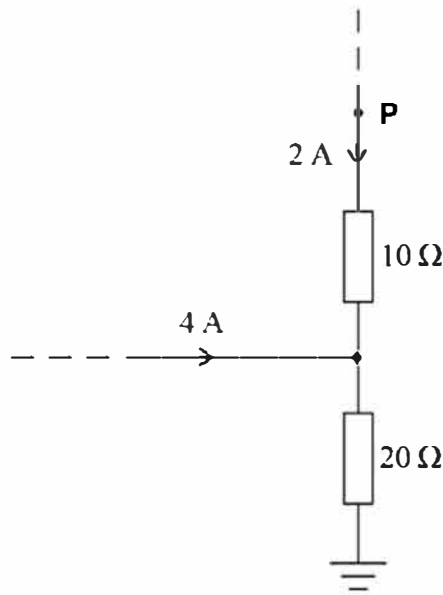


**2 3**

The diagram shows part of a circuit and the currents in the circuit.



What is the potential difference between point P and earth?

[1 mark]

A 60 V

B 100 V

C 120 V

D 140 V

**2 4**

A voltmeter has a resistance of  $4.0 \text{ k}\Omega$  and reads  $1.0 \text{ V}$  for every scale division on the meter.

A power supply of emf  $20 \text{ V}$  and negligible internal resistance is connected across this voltmeter and a resistor in series. The voltmeter reads two divisions.

What is the value of the resistor?

[1 mark]

A  $44 \text{ k}\Omega$


B  $36 \text{ k}\Omega$

C  $4.4 \text{ k}\Omega$

D  $3.6 \text{ k}\Omega$



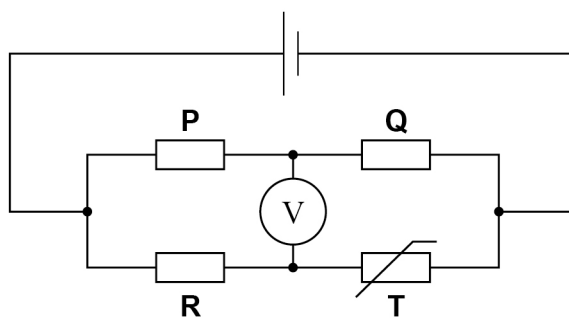**2 7** In the circuit below, the voltmeter reading is zero.



When the temperature of the thermistor **T** is increased, the voltmeter reading changes.

Which change to the circuit will restore the voltmeter to zero?


**[1 mark]**

- A** a reduction in the emf of the cell
- B** a reduction in the resistance of **P**
- C** an increase in the resistance of **Q**
- D** a reduction in the resistance of **R**



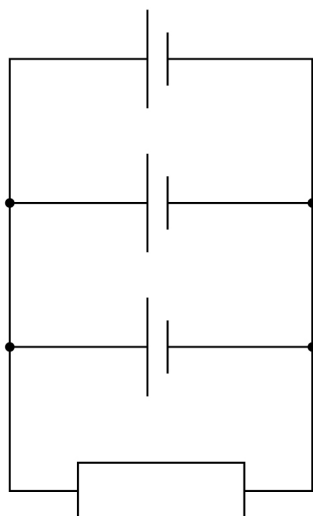**2 8**

A resistor of resistance  $R$  and three identical cells of emf  $E$  and internal resistance  $r$  are connected as shown.



What is the current in the resistor?

[1 mark]

**A**  $\frac{3E}{(3R+r)}$

**B**  $\frac{9E}{(3R+r)}$

**C**  $\frac{E}{R}$

**D**  $\frac{3E}{R}$


Turn over for the next question

Turn over ►



**2 9** In the circuit, the reading of the voltmeter is  $V$ .

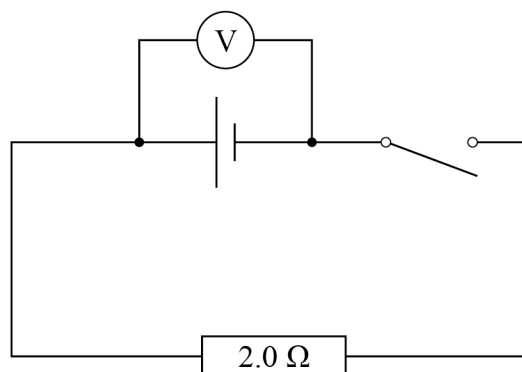When the switch is closed the reading becomes  $\frac{V}{3}$ .



What is the internal resistance of the cell?

[1 mark]

- A**  $0.33 \Omega$
- B**  $0.67 \Omega$
- C**  $4.0 \Omega$
- D**  $6.0 \Omega$

**END OF QUESTIONS**

