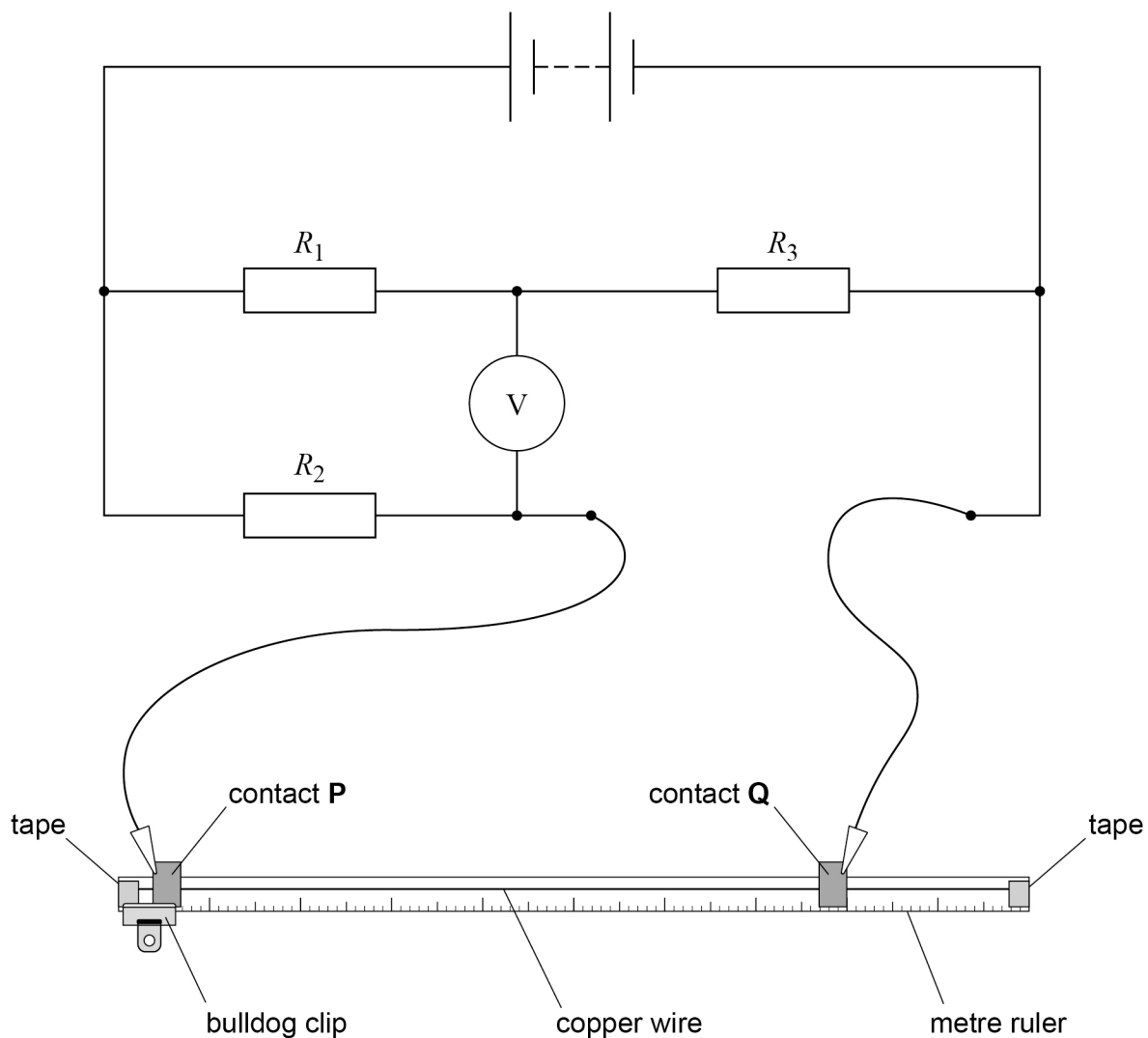


0 2

Figure 3 shows a circuit used to find the resistance per unit length of a copper wire.

Figure 3




The copper wire is fixed with tape to a metre ruler that has 2 mm graduations. Contact **P** is placed on the wire close to one end of the ruler and held firmly in place using a bulldog clip. When contact **Q** is placed on the wire as shown in **Figure 3** the voltmeter shows a non-zero reading.



Q is moved along the wire until the voltmeter reading is zero.

Figure 4 shows enlarged views of the position of **P** and the new position of **Q**.

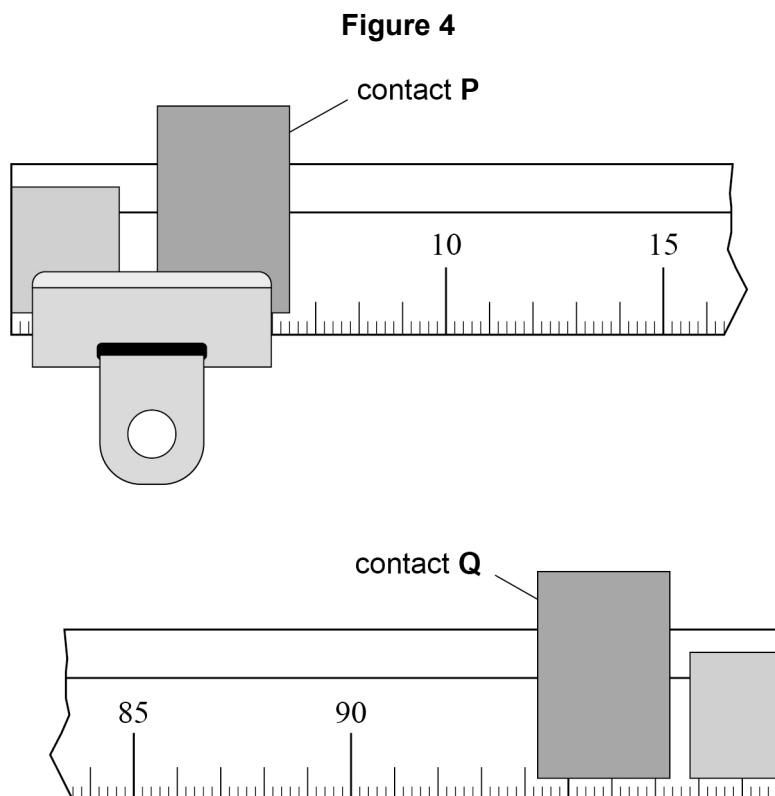

0 2 . 1 Determine, in m, the length x of copper wire between **P** and **Q**.

[1 mark]

$x =$ _____ m

Question 2 continues on the next page

Turn over ►



0 2 . 2 When the voltmeter reading is zero:

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

where R_4 is the resistance of the copper wire between **P** and **Q**.

Determine, in $\Omega \text{ m}^{-1}$, the resistance per unit length of the copper wire.

$$R_1 = 2.2 \text{ M}\Omega$$

$$R_2 = 3.9 \text{ k}\Omega$$

$$R_3 = 75 \Omega$$

[2 marks]

resistance per unit length = _____ $\Omega \text{ m}^{-1}$

0 2 . 3 The diameter d of the copper wire is approximately 0.4 mm.

Suggest:

- a suitable measuring instrument to accurately determine d
- how to reduce the effect of random error on the result for d .

[3 marks]



0 2 . 4 Determine the resistivity ρ of copper.

diameter d of the copper wire = 0.38 mm

[2 marks]

$\rho =$ _____ $\Omega \text{ m}$

The copper wire is replaced with a constantan wire of diameter 0.38 mm.

$$\frac{\text{resistivity of constantan}}{\text{resistivity of copper}} = 30$$

0 2 . 5 Suggest **one** change to the circuit to make the voltmeter read zero for the same value of x as in Question **02.1**.

[1 mark]

0 2 . 6 Calculate, in mm, the diameter of a constantan wire that has the **same** resistance per unit length as the copper wire.

[1 mark]

diameter = _____ mm

10

END OF SECTION A

Turn over ►



2 9

A wire is made from a material of Young modulus E .
The wire obeys Hooke's law.
The wire has an unstretched length L and a cross-sectional area A .
When a force is applied to the wire, the extension of the wire is e .

What is the elastic strain energy stored in the wire?

[1 mark]

A $\frac{AEe^2}{2L}$

B $\frac{L}{2Ae}$

C $\frac{Ae^2}{2EL}$

D $\frac{AEL}{2e}$

3 0

As the temperature of a copper wire increases, its resistance

[1 mark]

A remains constant.

B increases.

C decreases.

D remains constant at first and then decreases.

3 1

A $12\ \Omega$ resistor is connected across the terminals of a cell that has an emf of $2.0\ \text{V}$ and an internal resistance of $4.0\ \Omega$.

What is the terminal pd?

[1 mark]

A $0.50\ \text{V}$


B $0.75\ \text{V}$

C $1.30\ \text{V}$

D $1.50\ \text{V}$

Turn over ►

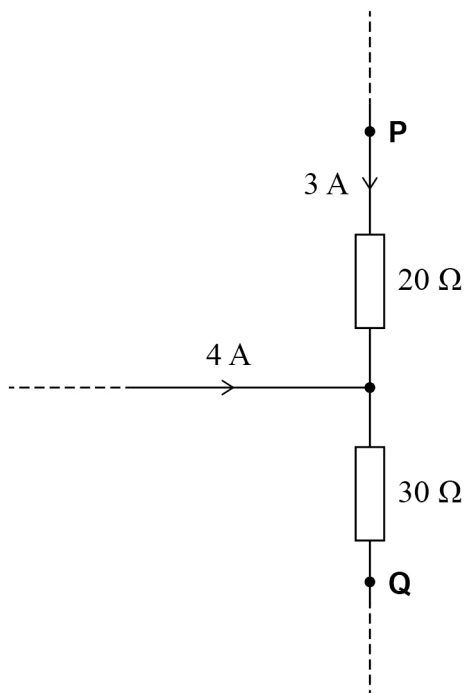3 2 The diagram shows the currents in part of a circuit.




What is the potential difference between points **P** and **Q**?

[1 mark]

- A** $60\ \text{V}$
- B** $70\ \text{V}$
- C** $180\ \text{V}$
- D** $270\ \text{V}$



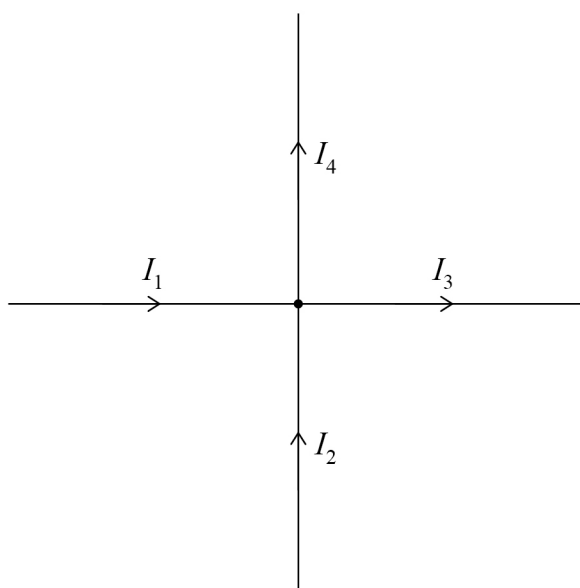3 3 The currents in the four wires obey the relationship $I_1 + I_2 + I_3 + I_4 = 0$



This relationship is an expression of the law of conservation of

[1 mark]

- A** charge.
- B** energy.
- C** potential difference.
- D** power.

3 4 A practical power supply provides a steady current I for a time t to an external circuit.

The emf of the power supply during t is equivalent to

[1 mark]

- A** the energy dissipated in the external circuit.
- B** the energy dissipated in the whole circuit.
- C** the energy dissipated in the whole circuit, divided by the product It .
- D** the potential difference across the terminals of the power supply.

30

END OF QUESTIONS




0 6 . 1

State what is meant by the emf (electromotive force) of a battery.

[1 mark]

Figure 10 shows the circuit diagram for a battery-powered torch.
The circuit contains three identical light emitting diodes (LEDs) and a resistor **R**.
The current in the circuit is 44 mA.

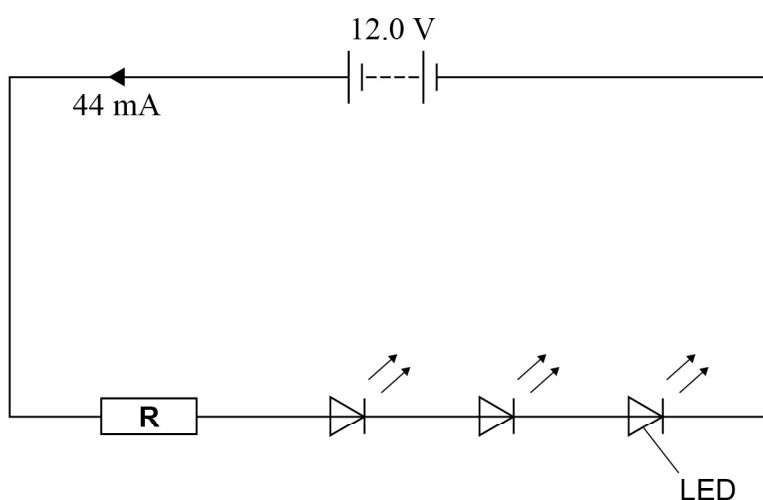Figure 10

0 6 . 2

Calculate the number of electrons that pass a point in the circuit in 37 minutes.


[2 marks]

number of electrons = _____

Question 6 continues on the next page**Turn over ►**

Figure 11 is the current–voltage characteristic for an LED used in the torch.

Figure 11

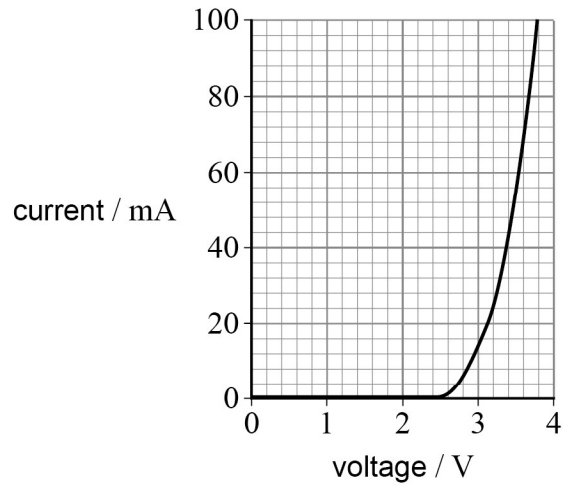

0 6 . 3 Determine the power output of one LED when the torch is on.

[3 marks]

power output = _____ W



The battery has an emf of 12.0 V and an internal resistance of 1.5 Ω .

0 6 . 4 Determine the resistance of **R** in **Figure 10**.

[4 marks]

resistance = _____ Ω

Question 6 continues on the next page


Turn over ►



0 6 . 5 Another appliance is connected to the battery as shown in **Figure 12**.

The current in the battery is 3.5 A when switch **S** is closed.

Figure 12

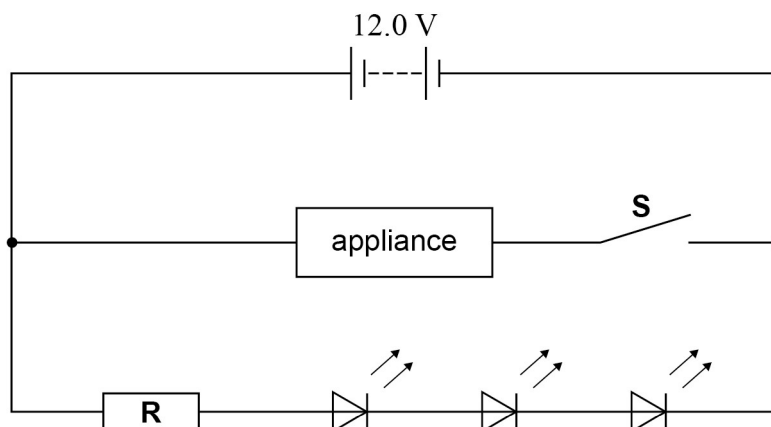

Each LED requires a voltage of at least 2.9 V to light.

Deduce whether the LEDs will light when **S** is closed.

[3 marks]

13

END OF QUESTIONS

