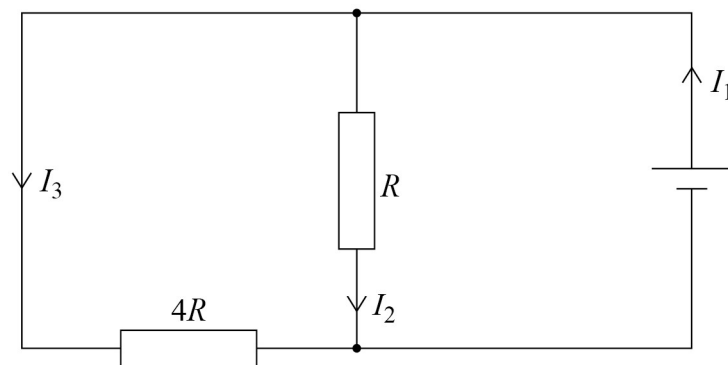


1 1

A cell with negligible internal resistance is connected to two resistors of resistance  $4R$  and  $R$ .

The currents  $I_1$ ,  $I_2$  and  $I_3$  in the circuit are shown.



Which equation is correct for this circuit?

[1 mark]

- A**  $I_1 = 4I_2$
- B**  $I_1 = 4I_3$
- C**  $I_2 = 4I_3$
- D**  $I_3 = 4I_1$


Turn over for the next question

Turn over ►



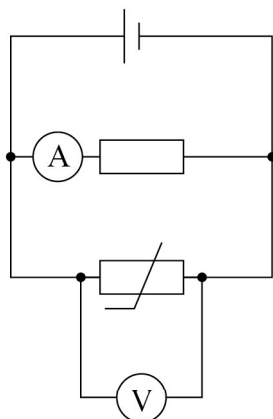**1 8**

A circuit contains a thermistor and a resistor in parallel. The internal resistance of the cell is negligible.



The temperature of the thermistor is increased.  
The temperature of the resistor is kept constant.

What is observed on the voltmeter and the ammeter?

**[1 mark]**

	Voltmeter reading	Ammeter reading	
<b>A</b>	decreases	increases	<input type="radio"/>
<b>B</b>	increases	increases	<input type="radio"/>
<b>C</b>	no change	increases	<input type="radio"/>
<b>D</b>	no change	no change	<input type="radio"/>

**Turn over ►**

**1 9**

The table shows the lengths and cross-sectional areas of two wires **X** and **Y** of the same metal.

Wire	Length / cm	Cross-sectional area / mm <sup>2</sup>
<b>X</b>	47	0.10
<b>Y</b>	23	0.40

The resistance of **X** is 6.0  $\Omega$ .

The temperature of **Y** is the same as the temperature of **X**.

What is the resistance of **Y**?

**[1 mark]**





**A** 0.12  $\Omega$

**B** 0.73  $\Omega$




**C** 1.2  $\Omega$

**D** 3.1  $\Omega$

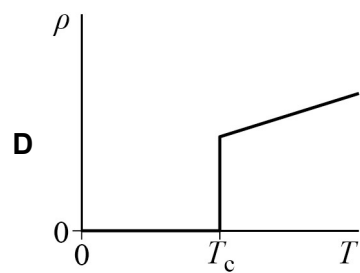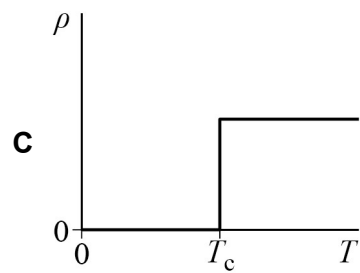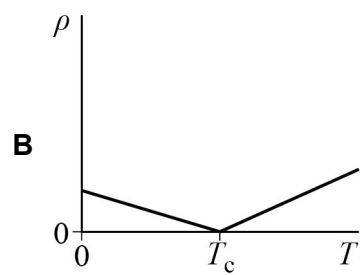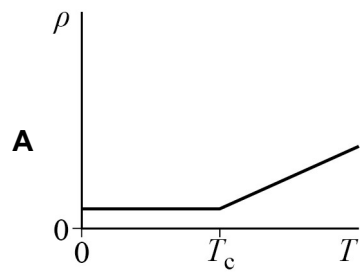

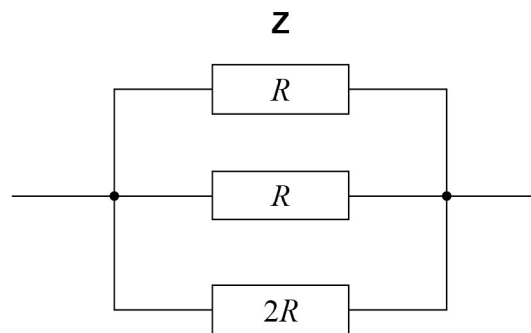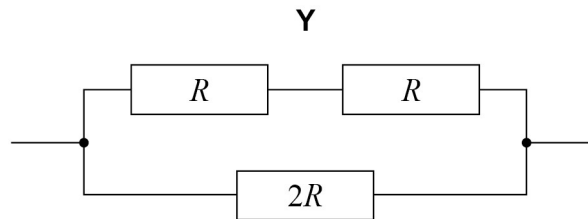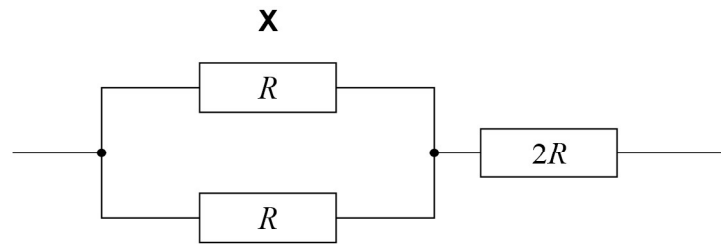**2 0**A superconducting material has a critical temperature  $T_c$ .Which graph shows the variation of resistivity  $\rho$  with temperature  $T$ ?**[1 mark]****Turn over ►**

**2 1** X, Y and Z are three networks of resistors.



Which gives the networks in order of largest total resistance to smallest total resistance?

**[1 mark]**

- A** X, Y, Z
- B** Y, X, Z
- C** Z, X, Y
- D** Z, Y, X



What is the Young modulus of the material?

[1 mark]

A  $1.2 \times 10^5$  Pa

B  $1.5 \times 10^5$  Pa

C  $1.2 \times 10^{11}$  Pa

D  $1.5 \times 10^{11}$  Pa

**2 8** Which row shows the resistance of an ideal ammeter and of an ideal voltmeter?

[1 mark]

	Resistance of ammeter	Resistance of voltmeter	
<b>A</b>	zero	zero	<input type="checkbox"/>
<b>B</b>	zero	infinite	<input type="checkbox"/>
<b>C</b>	infinite	zero	<input type="checkbox"/>
<b>D</b>	infinite	infinite	<input type="checkbox"/>

**2 9** The current in a resistor is 15 mA.

How many electrons pass through the resistor in 3 minutes?

[1 mark]

A  $2.8 \times 10^{17}$

B  $1.7 \times 10^{19}$

C  $2.8 \times 10^{20}$


D  $1.7 \times 10^{22}$

Turn over ►



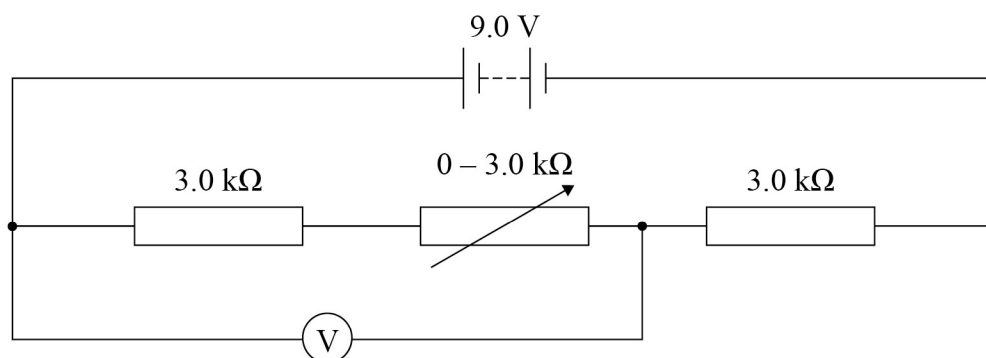**3 0**

Three resistors are connected in series with a 9.0 V battery of negligible internal resistance.



The resistance of the variable resistor is varied from 0 to  $3.0 \text{ k}\Omega$ .

The range of potential difference observed on the voltmeter is

**[1 mark]**





- A** 0 to 6.0 V
- B** 3.0 V to 6.0 V
- C** 4.5 V to 6.0 V
- D** 4.5 V to 9.0 V



**3 1**

The current–voltage characteristic between 0 and 6.0 V is required for a filament lamp. The lamp is connected in a circuit with a battery of emf 6.0 V and negligible internal resistance.

Which circuit should be used?

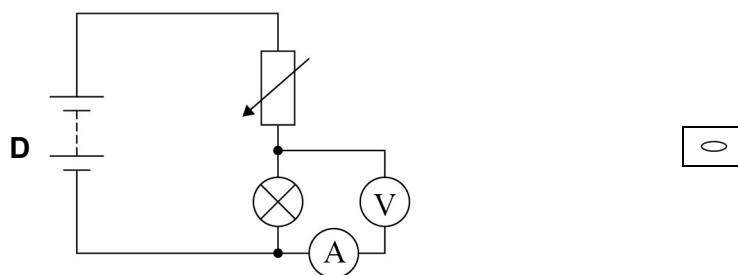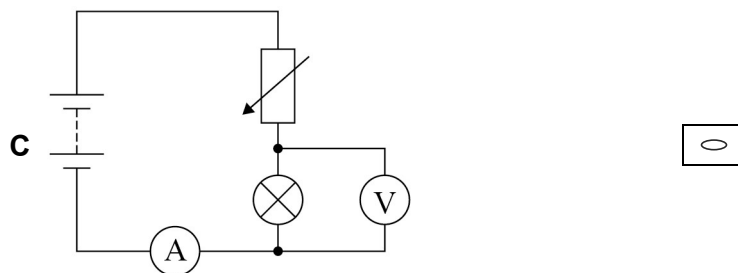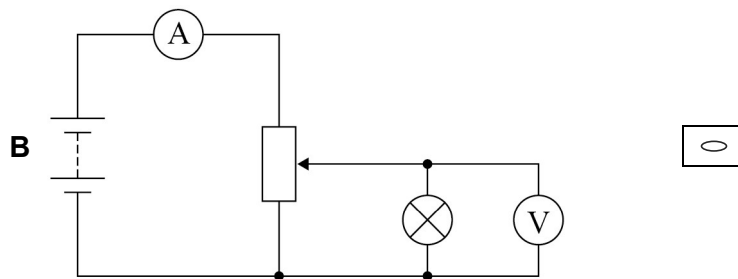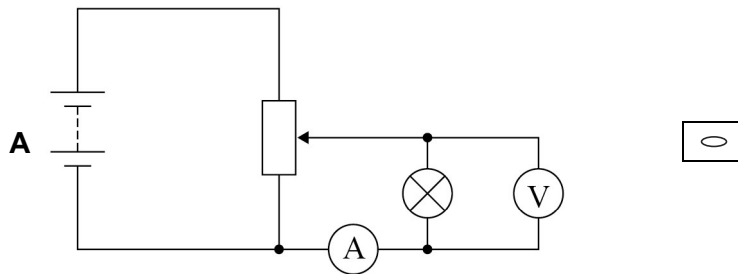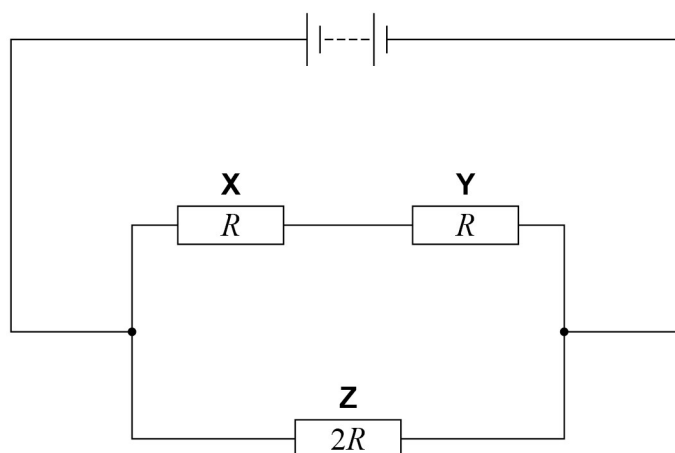
**[1 mark]**

Turn over ►





- 3 2** The diagram shows a circuit containing three resistors **X**, **Y** and **Z**.



**X** and **Y** each have resistance  $R$ .  
**Z** has resistance  $2R$ .

What is  $\frac{\text{power in X}}{\text{power in Z}}$ ?

[1 mark]

- A**  $\frac{1}{4}$
- B**  $\frac{1}{2}$
- C** 2
- D** 4

- 3 3** A pellet of mass 25 g travelling horizontally at  $40 \text{ m s}^{-1}$  enters a fixed wooden block. The pellet stops after travelling a horizontal distance of 2.5 cm in the block.

What is the average resistive force acting on the pellet?

[1 mark]

- A** 20 N
- B** 800 N
- C** 1600 N
- D** 8000 N

