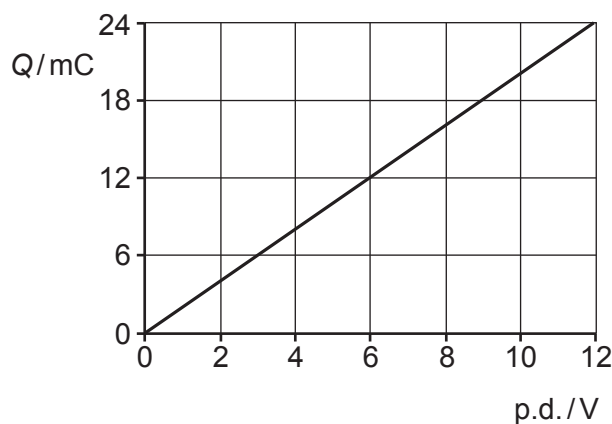


The following information is for use in questions 7 and 8.

The diagram shows the $Q - V$ graph for a capacitor charged to 12V.



$$Q = CV$$

$$C = \frac{Q}{V} = \frac{24 \text{ mC}}{12}$$

$$2 \text{ mF}$$

7 What is the capacitance?

- A $2 \times 10^{-3} \text{ F}$
- B $144 \times 10^{-3} \text{ F}$
- C $288 \times 10^{-3} \text{ F}$
- D 500 F

$$E = \frac{1}{2} QV = \frac{1}{2} \times 24 \text{ m} \times 12$$

$$= 144 \times 10^{-3} \text{ J}$$

Your answer

[1]

8 Which of the following is the energy stored?

- A $2 \times 10^{-3} \text{ J}$
- B $144 \times 10^{-3} \text{ J}$
- C $288 \times 10^{-3} \text{ J}$
- D 500 J

Your answer

[1]

- 34 A student makes an iterative model for the decay of charge on a capacitor. The time constant of the circuit is $RC = 10\text{s}$.

time lapsed /s	charge Q on capacitor /C	charge ΔQ leaving capacitor in time interval $\Delta t = 1\text{s}$ /C	charge Q remaining after time interval Δt /C
t	Q	$\Delta Q \approx \frac{Q\Delta t}{RC}$	$Q = (Q - \Delta Q)$
0	5	$\frac{5 \times 1}{10} = 0.5$	$5 - 0.5 = 4.5$
1	4.5	$\frac{4.5 \times 1}{10} = 0.45$	$4.5 - 0.45 = 4.05$

- (a) Complete the numerical values in the two blank cells in the table. [2]

- (b) (i) Explain the physics behind the approximation in the third column of the table $\Delta Q \approx \frac{Q\Delta t}{RC}$.

change in ΔQ in time t (or Δt) = $I \times \Delta t$
 $V = IR \Rightarrow \Delta Q = \frac{V}{R} \Delta t$. $Q = CV$ so $V = \frac{Q}{C}$
 $\therefore \Delta Q = \frac{Q \Delta t}{RC}$
 It's approx $\because I$ changes during Δt [2]

- (ii) State the assumption made in using this approximation and explain how its effect can be made insignificant.

that I is constant (or V , or Q or cap) during Δt ... which it isn't. Reduce Δt to a smaller value [2]

- 2 This question is about charging a capacitor in a circuit with two resistors in series.

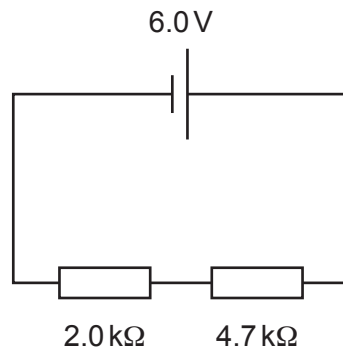


Fig. 2.1

- (a) Show that the p.d. across the 4.7 kΩ resistor in the circuit in Fig. 2.1 is about 4V, assuming that the cell has zero internal resistance.

$$\left(\frac{4.7}{2 + 4.7} \right) \times 6 = \underline{\underline{4.20}}$$

[2]

- (b) A student changes the circuit as shown in Fig. 2.2

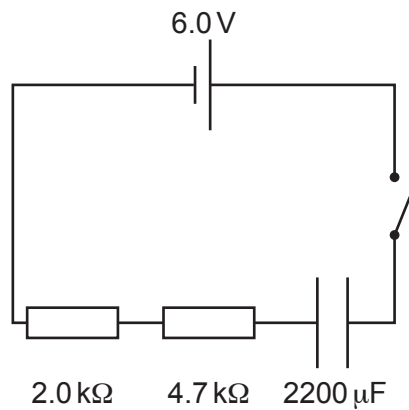


Fig. 2.2

Show that the time constant of the circuit is about 15s.

$$\begin{aligned} \tau = RC &= 2200 \times 10^{-6} \times 2000 \times 4700 \\ &= \underline{\underline{14.7 \text{ s}}} \end{aligned}$$

[2]

- (c) The graph in Fig. 2.3 shows how the p.d. across the capacitor varies with time up to $5RC$. Add a line to the graph that shows how the p.d. across the **4.7 kΩ resistor** varies with time.

Add another line to show how the p.d. across the **2.0 kΩ resistor** varies with time. Label the lines.

max V over 4.7k = 4.2
 max V across 2kΩ with k ≈ 1.8

both exp → 0 at 5RC

had to draw on pc

Your lines must be better than mine!

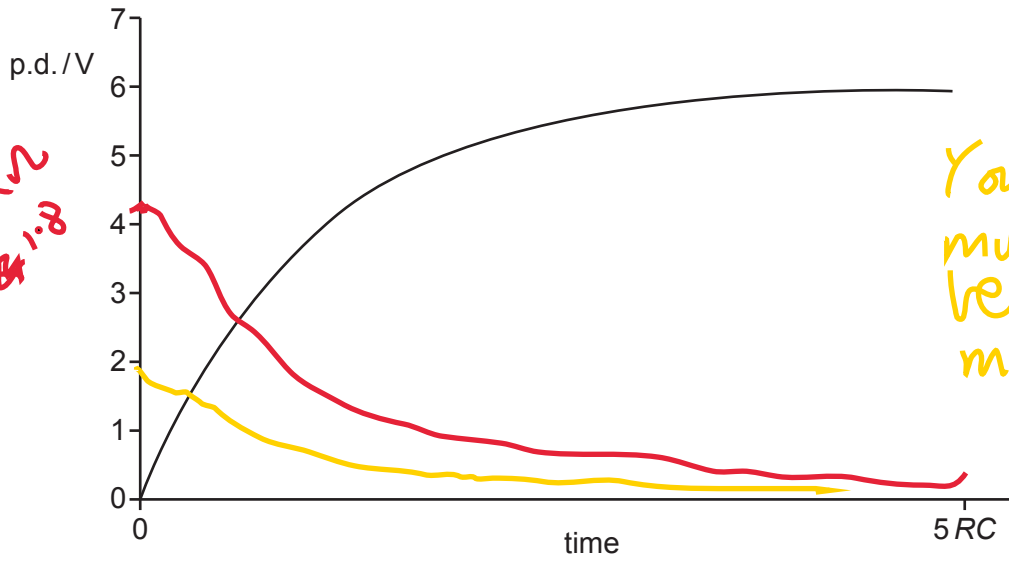


Fig. 2.3

[2]

- (d) Calculate the time it takes from the start of the charging for the p.d. across the capacitor to reach 5.0V.

$$V = V_0(1 - e^{-t/RC}) \Rightarrow \frac{V}{V_0} = 1 - e^{-t/RC} \quad \ln 1 = 0$$

$$\frac{V}{V_0} - 1 = -e^{-t/RC} \Rightarrow 1 - \frac{V}{V_0} = e^{-t/RC}$$


$$\Rightarrow \ln\left(1 - \frac{V}{V_0}\right) = -\frac{t}{RC} \Rightarrow -1.79 \times RC = -t$$

26.3 sec

time = s [4]

The following information is for use in questions 13 and 14.

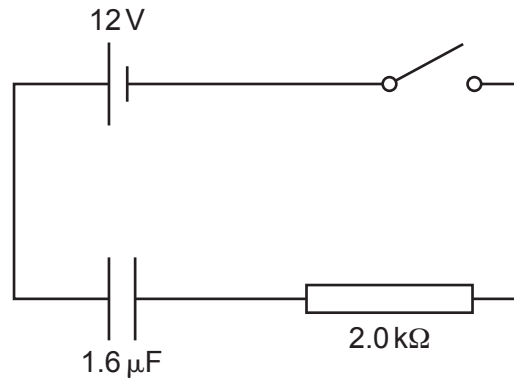An uncharged capacitor and a resistor are connected in this circuit.



	current/mA	p.d. across the capacitor/V	p.d. across the resistor/V
A	0	12	0
B	2	8	4
C	3	6	6
D	6	0	12

- 13 Which set of values **A** to **D** above, most closely represents the situation immediately after the switch is closed?

no p.d. over C

Your answer

D

[1]

- 14 Which set of values **A** to **D** above, most closely represents the situation 3 seconds after the switch is closed?

Your answer

A

$$RC = 1.6 \times 10^{-6} \times 2 \times 10^3$$

$$= 3.2 \times 10^{-3} \text{ s}$$

*so its a fully
Charge Capacitor*

*so I ≈ 0 amp
& V_C = 12V*

[1]